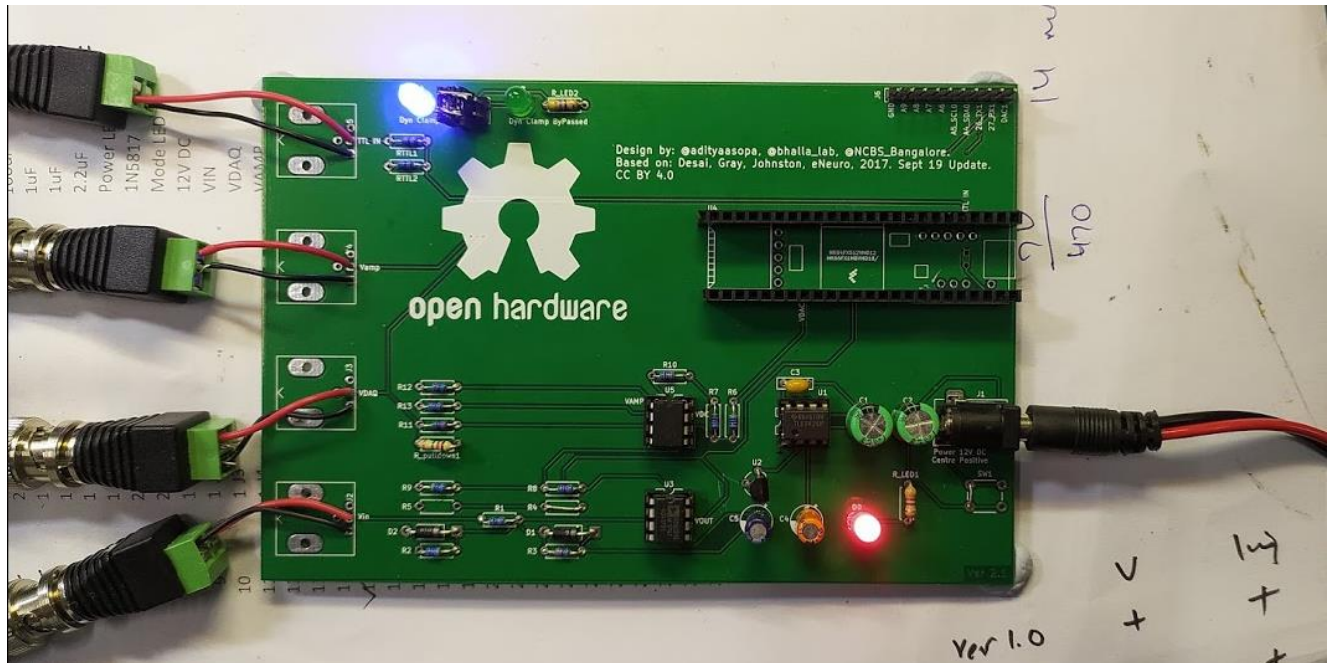


Dynamic Clamp 2.0: Calibration and Setup

Aditya Asopa, Bhalla Lab, NCBS

Oct 2020



General Points:	3
Circuit Schematic	4
Stages	6
Testing on Bench	7
Stage 1: Voltage rails.	7
Stage 2: 3.3V Voltage rail	7
Stage 3: Vin -> Vout scaling by AD8031	7
Stage 5a: Testing the scaling of VDAC to VDC	8
Stage 5b: Adding VDC to VDAQ	8
Testing the Stagewise IO Relationship/Scaling Using an Oscilloscope	11
Stage 3: AD8031 Vin --> Vout	11
Stage 5a: LM358a, VDAC+VDAQ --> VAMP, with VDAQ = 0	13
Stage 5b: VDAQ + VDAC --> VAMP, with VDAC = 0	15
Theoretical Calibration	17
Input Stage Calibration	17
Output Stage Calibration	19
Direct Calibration with a Function Generator and an Oscilloscope	21
Calibration with a Model Cell Using Processing	24
Input Stage calibration with Processing Program	25
Output stage calibration with Processing Program	25
Solution: Output stage calibration with a Script	27
Alternative Calibration with a Teensy Program	30
Conclusion	32
Feeding the calibration values in Dynamic Clamp	33
Appendix	35
Script for alternative calibration using a Teensy program	35
Bonus method to solve the output calibration problem with the processing calibration program	37

General Points:


Testing the board


- Do not keep loose metal items on the bench around the board. They can short contacts.
- Keep the board fixed at one place, with blue tack or foam.
- Keep the benchtop tidy.
- Do not touch ICs with bare hands without grounding.
- Be careful around the capacitors even after the power supply is disconnected.
- Always disconnect power supply to the board before changing anything.
- Do not put Teensy before testing all the other stages.

Equipment Needed

- Oscilloscope
- Function Generator (extra good if saw tooth function present, we are going to make good use of it)
- Computer with Processing, Teensy and Arduino IDE installed.
- Breadboard Jumpers
- Alligator ended BNCs
- Bench top power supply ($\pm 10\text{V}$ range)

Circuit Schematic

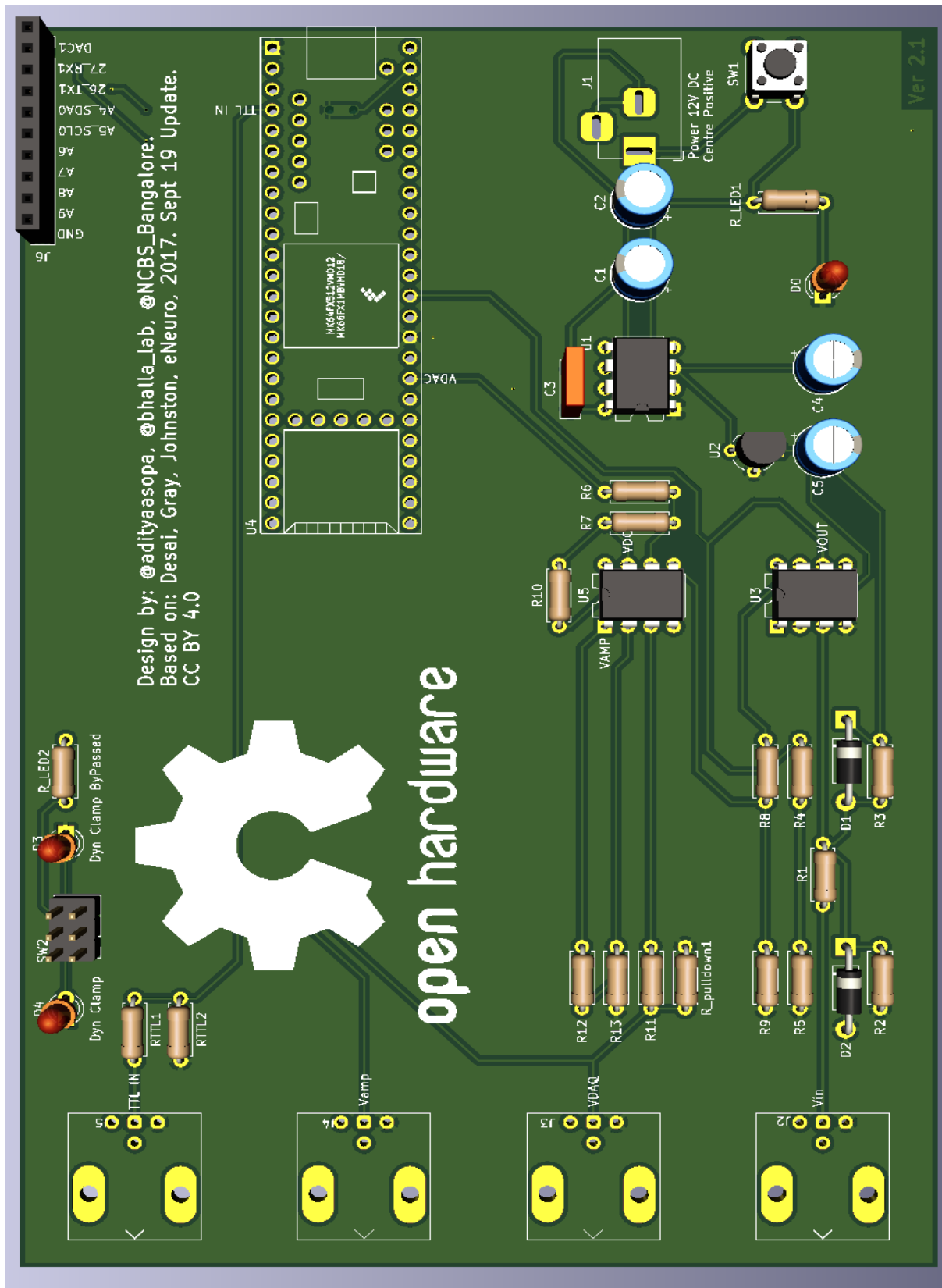

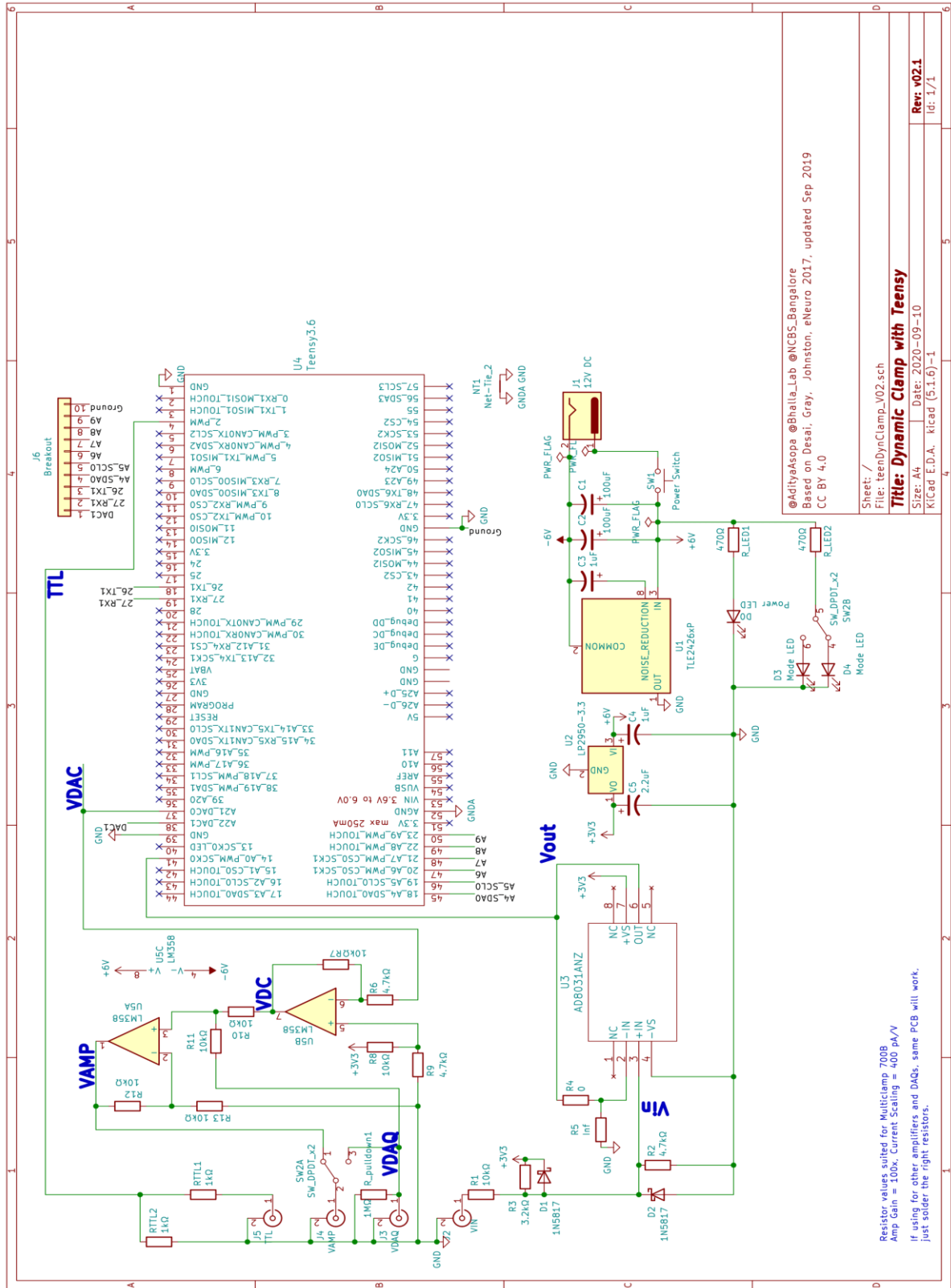

Stages

Stage	Chip	Function	Input Signal(s)	Output Signals												
1	TLE2426	Rail Splitter, create a rail exactly the centre of supply voltage range	+/- V_{supply} (9 to 24V)	(+V/2) to Gnd to (-V/2)												
2	LP2950-33	3.3V regulator	+V/2 to Gnd	3.3V to Gnd												
3	AD8031	Amplifier: scales patch amplifier readout of membrane voltage into teensy acceptable range	V_{in} Vin is cell voltage V_m amplified by the patch amplifier. (For axon, gain = 100x) V_m range = ± 100 mV after 100x gain: V_{in} range = ± 10 V	V_{out} <table><tr><td></td><td>Vin</td><td>Vout</td></tr><tr><td>Max</td><td>+10V</td><td>3.3V</td></tr><tr><td>zero</td><td>0 V</td><td>1.65 V</td></tr><tr><td>Min</td><td>-10V</td><td>0 V</td></tr></table>		Vin	Vout	Max	+10V	3.3V	zero	0 V	1.65 V	Min	-10V	0 V
	Vin	Vout														
Max	+10V	3.3V														
zero	0 V	1.65 V														
Min	-10V	0 V														
4	Teensy 3.6	Computing conductances, producing scaled outputs for current injection	V_{out}	V_{DAC}												
5	LM358	Amplifier: produces voltage proportional to the current to be injected in the cell 5a. scales V_{DAC} to V_{DC} 5b. Add V_{DAQ} to V_{DC}	V_{DAC} signal range: 3.3 - 0 V V_{DC} and V_{DAQ}	V_{DC} range: -3V to +3V $V_{AMP} = V_{DC} + V_{DAQ}$												

The dynamic clamp circuit does not read the membrane potential of the cell directly but reads an amplified copy of it that is generated by the patch clamp amplifier. This amplification gain is kept at 100mV/V. Once calibrated, this gain should not be changed when the dynamic clamp circuit is in operation. For that reason, it is recommended that this signal be taken from secondary output of Multiclamp amplifier. This will allow us to record the membrane potential of the cell at any gain using primary output independent of the dynamic clamp.

V_{AMP} is a voltage that is sent to the patch clamp amplifier that then injects a proportional amount of current into the patched cell. This proportionality constant can be changed in multiclamp. Usually it is set to 400pA/V. This means that if V_{AMP} is 1 V, the patch clamp amplifier will inject 400 pA into the cell.

Testing on Bench

Stage 1: Voltage rails.

- Bench top power supply was used.
- Connect the power supply.
- Measure voltage across the power supply jack: 18 V
- Across pin 1 of rail splitter (TLE2426) and both terminals of power supply jack: +9 V and -9 V
- Measure voltage at pin 4 w.r.t GND: -9 V
- Measure voltage at pin 8 w.r.t GND: +9 V

Stage 2: 3.3V Voltage rail

- Measure the voltage at pin 1 of LP2950 with respect to GND: 3.30 V
- Measure the voltage at pin 7 of AD8031 with respect to GND: 3.30 V
- Measure the voltage at D1: 3.30 V

Stage 3: $V_{in} \rightarrow V_{out}$ scaling by AD8031

- Give a linear ramp of voltage from -1 V to +1 V using a function generator at V_{in} BNC.
- Measure V_{out} with oscilloscope using a jumper probe put into pin 12 of Teensy socket (without Teensy present) or a probe touched to pin 6 of AD8031.

Fig. V_{in} shown in yellow (-10 to +10V) and V_{out} (0 to 3.3 V) shown in green, perfectly linear scaling as expected



Stage 5a: Testing the scaling of VDAC to VDC

- Put the function generator input into VDAC pin of teensy socket w.r.t. GND.
- Input function should be a ramp from 0 to 3.3V, in the range the Teensy would generate.
- Measure output of first opAmp of LM358 pin 7 w.r.t ground.


Fig. VDAC in yellow (0.08 to 3.36 V) and VDC (6.6 to 7.4 V) in green showing linear scaling.



Stage 5b: Adding VDC to VDAQ

- VDAQ is the voltage that comes from the DAQ as the scaled version of command current that is going to be injected into the cell by the amplifier. We want to add our VDC (dynamic clamp scaled voltage) to it.
- Give an analogue signal at VDAQ (BNC terminal on board) while giving another signal at VDAC (Pin 8 of teensy socket).
- Measure the resultant signal VAMP at VAMP BNC terminal or at the mode jumper terminal.

Fig. $VAMP = VDC + VDAQ$. Linear and inverted scaling of VDAC (0 to 3.3 V, yellow) to VDC (-3.7 to 3.3 V, pink), with VAMP (-3.6 to 3.3 V, green), when $VDAQ = 0$.

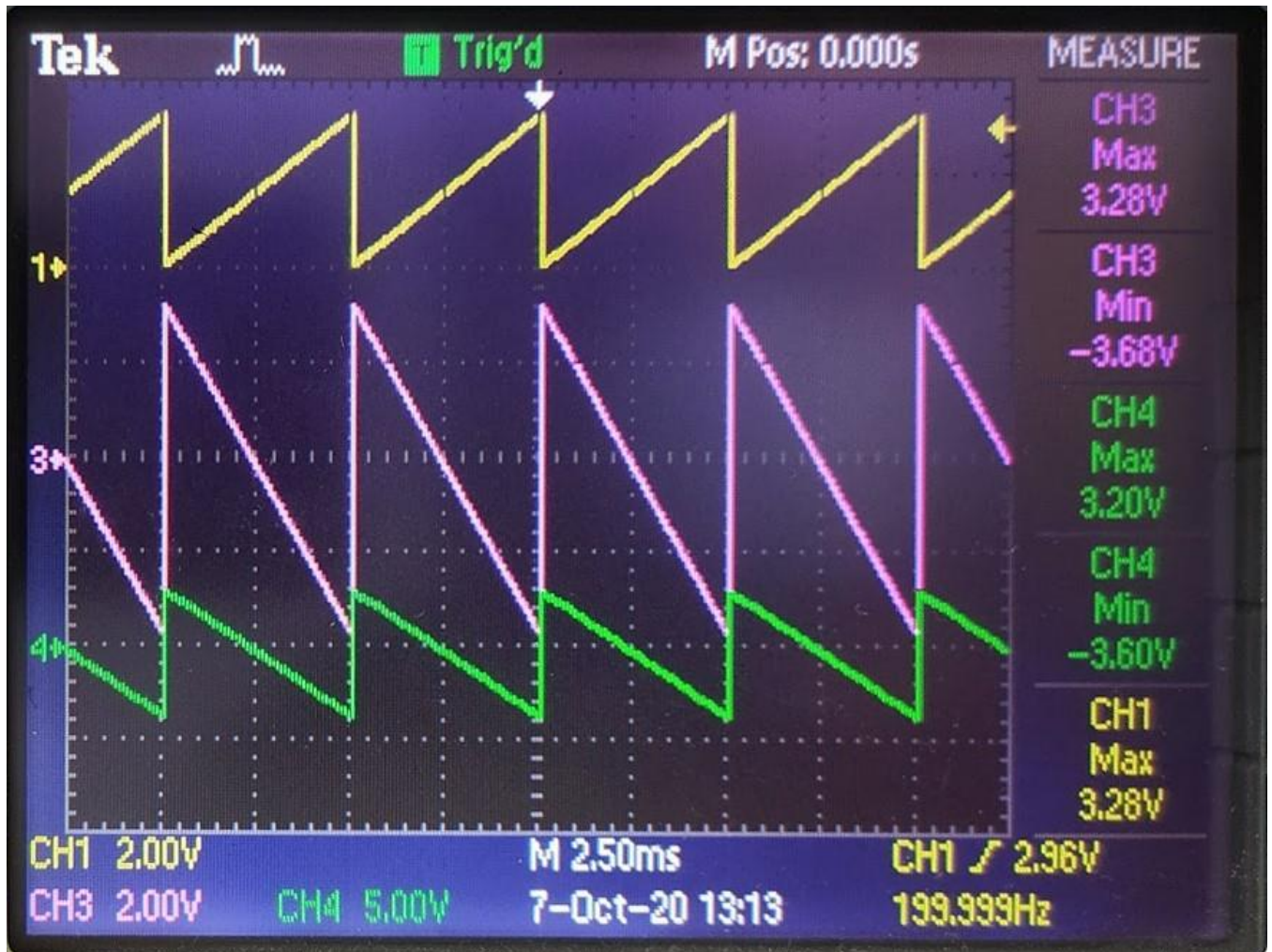

- Now turn VDAC to be zero and supply a voltage signal at VDAQ. Read output at VDC and VAMP.
- As VDAC is zero, VDC should be zero too, and VAMP should just be a scaled version of VDAQ signal.

Fig. VDAC is zero (yellow) and a signal is supplied at VDAQ (blue, 0 to 3 V). As a result VDC is zero and VAMP is a linearly scaled signal proportional to VDAQ.



These quick tests show that the relationship between different signals, their ranges, scaling, and inversions are as expected.

Testing the Stagewise IO Relationship/Scaling Using an Oscilloscope

These tests are done to test the individual modules or stages of the dynamic clamp circuit on the board. Please refer to the circuit schematic for labels and naming conventions.

Stage 3: AD8031 Vin --> Vout

Theoretical relation:

$$V_{OUT} = \frac{\frac{V_{IN}}{R_1} + \frac{3.3}{R_3}}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)} \quad (1)$$

or

$$V_{OUT} = \frac{1}{R_1} \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right) * V_{IN} + \frac{1}{R_3} \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right)$$

Given: $R_1 = 22k\Omega$, $R_2 = 10k\Omega$, $R_3 = 3.2k\Omega$

$$V_{OUT} = 0.15993 * V_{IN} + 1.6493 \quad (2)$$

Here:

$$m_{in} = \frac{1}{R_1} \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right) = 0.15993 \quad (2a)$$

And


$$c_{in} = \frac{1}{R_3} \left(\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right) = 1.6493 \quad (2b)$$

Setup:

Use a function generator to produce voltage levels and feed it to V_{in} and measure V_{out} using an oscilloscope.

Measurement: Table 1

Vin (V)	Expected Vout (V)	Observed Vout (V)	Error
	$V_{OUT} = 0.15993 * V_{IN} + 1.6493$		
-9.940	0.060	0.068	-14.102
-7.930	0.381	0.403	-5.759
-5.940	0.699	0.716	-2.386
-3.920	1.022	1.040	-1.724
-2.000	1.329	1.360	-2.299
0.041	1.656	1.680	-1.458
2.100	1.985	2.000	-0.748
4.070	2.300	2.320	-0.860
6.150	2.633	2.650	-0.651
8.040	2.935	2.990	-1.869
10.100	3.265	3.290	-0.778
Slope (m_{in})	0.1599	0.1609	
Intercept (c_{in})	1.6493	1.6721	

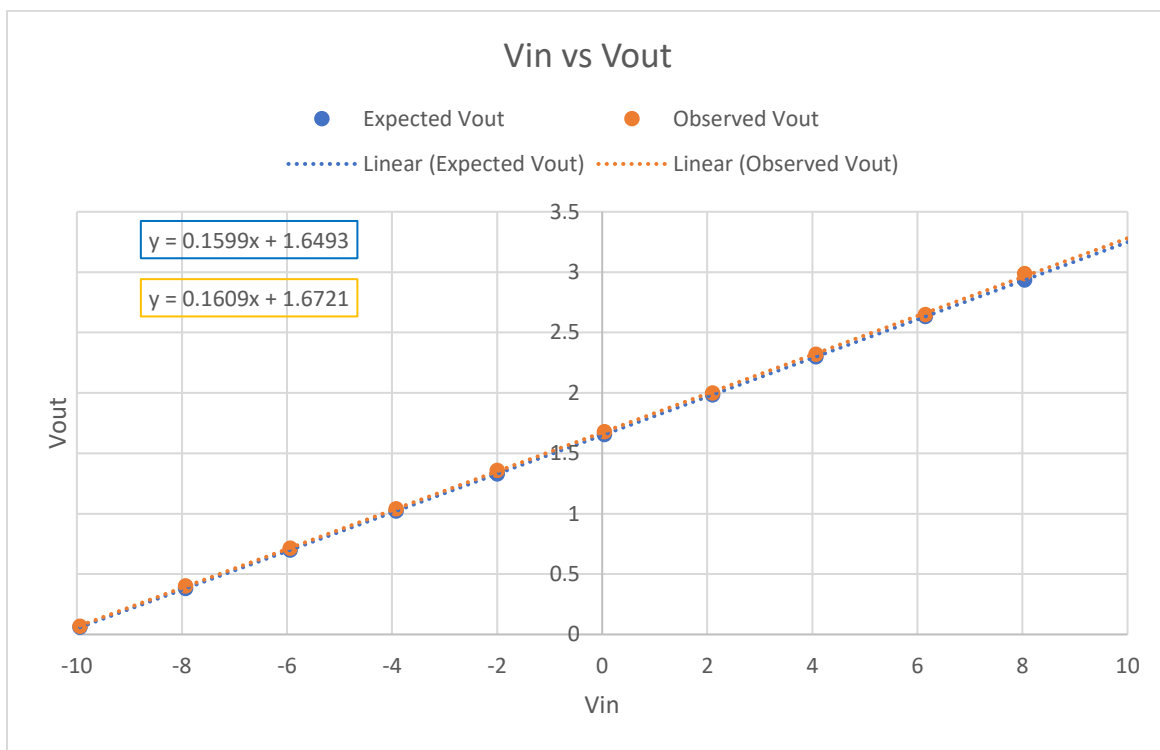

Stage 5a: LM358a, VDAC+VDAQ --> VAMP, with VDAQ = 0

Theoretical relation:

$$V_{DC} = -V_{DAC} * \frac{R_7}{R_6} + 3.3 * \left(\frac{R_9}{R_8 + R_9} \right) \left(\frac{R_6 + R_7}{R_6} \right) \quad (4)$$

Given: $R_6 = 4.7k\Omega$, $R_7 = 10k\Omega$, $R_8 = 10k\Omega$, $R_9 = 4.7k\Omega$

$$V_{DC} = -2.1277 * V_{DAC} + 3.3$$

Here:

$$m_{out} = \frac{R_7}{R_6} = -2.1277 \quad (4a)$$

And

$$c_{out} = 3.3 * \left(\frac{R_9}{R_8 + R_9} \right) \left(\frac{R_6 + R_7}{R_6} \right) = 3.3 \quad (4b)$$

And

$$V_{AMP} = V_{DAQ} + V_{DC}$$

$$V_{AMP} = V_{DAQ} - 2.1277 * V_{DAC} + 3.3 \quad (5)$$

If VDAQ is GND i.e., 0 V


$$V_{AMP} = V_{DC} = -2.1277 * V_{DAC} + 3.3$$


Setup:

Feed voltage using a function generator (for ex, using a very low frequency square pulse), to VDAC, and connect VDAQ to Gnd (0 V) and measure using a function generator at VAMP.

Measurement: Table 2

VDAQ	VDAC	Expected VDC $= -2.1277 * V_{DAC} + 3.3$	Observed VDC	VDC Error	Expected VAMP $= -2.1277 * V_{DAC} + 3.3$	Observed VAMP	VAMP Error
0.000	0.043	3.209	3.400	-5.940	3.209	3.360	-4.694
0.000	0.236	2.798	2.980	-6.510	2.798	2.930	-4.722
0.000	0.442	2.360	2.560	-8.494	2.360	2.510	-6.375
0.000	0.638	1.943	2.170	-11.709	1.943	2.070	-6.561
0.000	0.840	1.513	1.640	-8.411	1.513	1.650	-9.072
0.000	1.040	1.087	1.220	-12.211	1.087	1.250	-14.971
0.000	1.240	0.662	0.814	-23.016	0.662	0.821	-24.074
0.000	1.640	-0.189	-0.005	97.360	-0.189	-0.032	83.101
0.000	2.040	-1.040	-0.901	13.401	-1.040	-0.884	15.035
0.000	2.430	-1.870	-1.620	13.379	-1.870	-1.740	6.962
0.000	3.040	-3.168	-2.970	6.253	-3.168	-3.040	4.043
0.000	3.240	-3.594	-3.390	5.666	-3.594	-3.460	3.718
Slope		-2.128	-2.120		-2.128	-2.131	
Intercept		3.300	3.472		3.300	3.449	

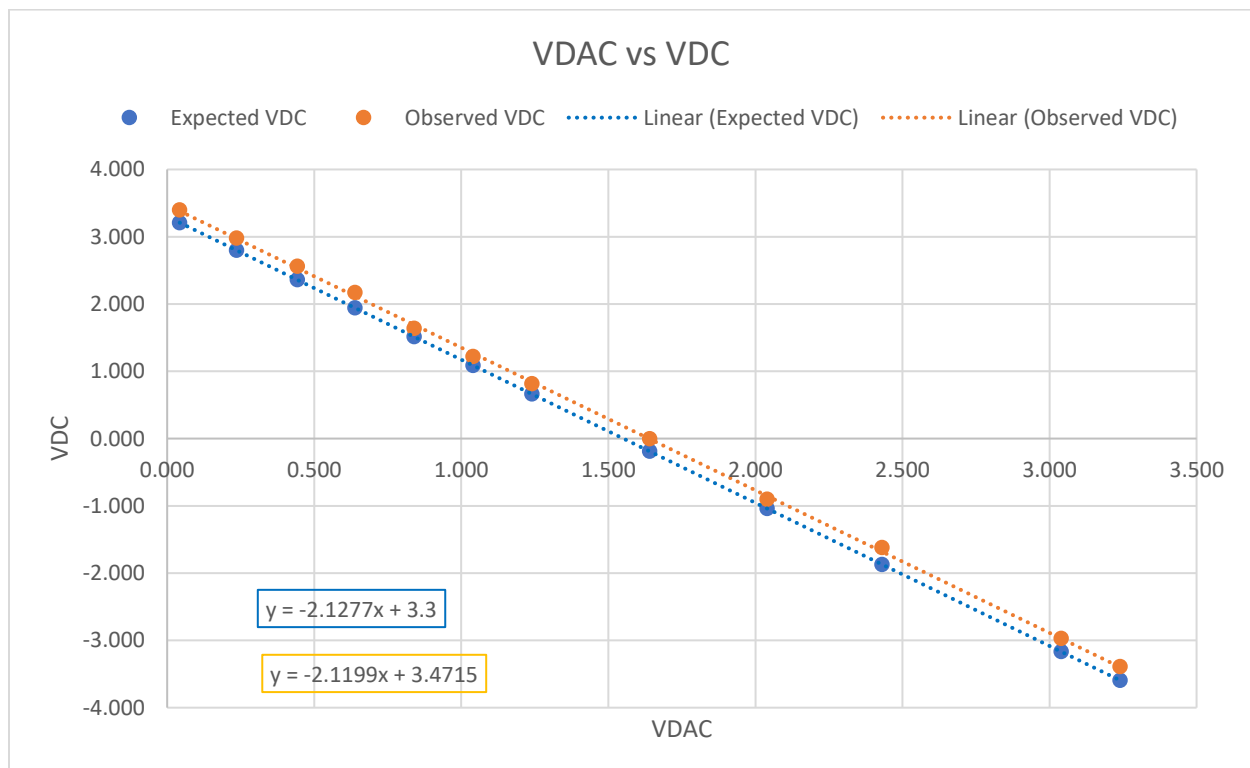

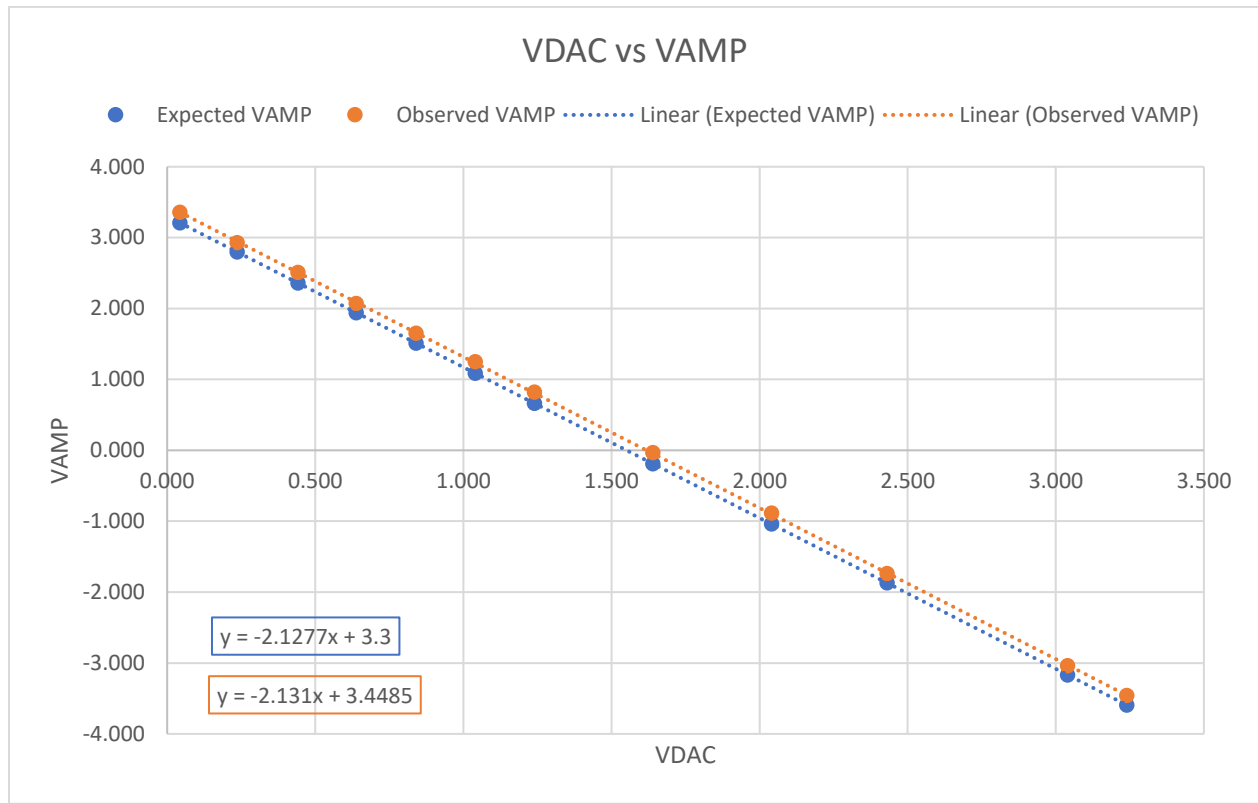

Stage 5b: VDAQ + VDAC --> VAMP, with VDAC = 0

Theoretical relation:

From Eq 4

$$V_{AMP} = V_{DAQ} - 2.1277 * V_{DAC} + 3.3$$

If VDAC is GND i.e., 0 V


$$V_{AMP} = V_{DAQ} + 3.3$$

Setup:

Now switch the function generator to input into VDAQ and connect VDAC to Gnd (0 V) and measure from VAMP.

Measurement: Table 3

VDAQ	VD AC	Expected VDC $= V_{DAQ} - 2.1277 * V_{DAC} + 3.3$	Observed VDC	VDC Error	Expected VAMP $= V_{DAQ} - 2.1277 * V_{DAC} + 3.3$	Observed VAMP	VAMP Error
-2.960	0.0	3.300	3.410	-3.333	0.340	0.395	16.176
-2.360	0.0	3.300	3.410	-3.333	0.940	1.000	-6.383
-1.560	0.0	3.300	3.410	-3.333	1.740	1.800	-3.448
-1.160	0.0	3.300	3.410	-3.333	2.140	2.200	-2.804
-0.766	0.0	3.300	3.410	-3.333	2.534	2.600	-2.605
-0.369	0.0	3.300	3.410	-3.333	2.931	3.000	-2.354
0.040	0.0	3.300	3.410	-3.333	3.340	3.400	-1.796
0.444	0.0	3.300	3.410	-3.333	3.744	3.780	-0.962
1.040	0.0	3.300	3.410	-3.333	4.340	4.380	-0.922
1.640	0.0	3.300	3.410	-3.333	4.940	4.960	-0.405
2.040	0.0	3.300	3.410	-3.333	5.340	5.360	-0.375
3.050	0.0	3.300	3.410	-3.333	6.350	6.360	-0.157
Slope		0.000	0.000		1.000	0.991	
Intercept		3.300	3.410		3.300	3.346	

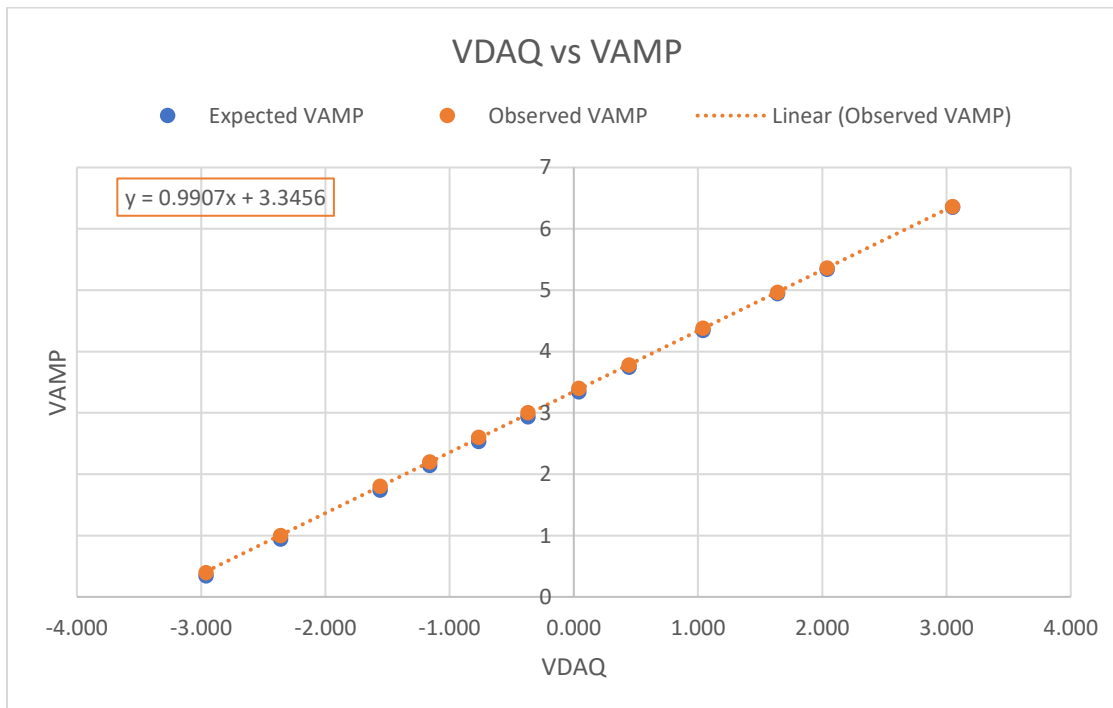

Theoretical Calibration

Calibration sets the relationship between amplifier and Teensy.

Input stage: relation between cell membrane voltage (V_m in mV) and the ADC values read by Teensy.

Output stage: relation between DAC values sent by Teensy and current injected by the amplifier into the cell.

Input Stage Calibration

V_{in} i.e., V_m after amplification by multiclamp:

$$V_{in} = V_m * g_{in}$$

V_{out} produced by AD8031, from Eq. 2:

$$V_{out} = m_{in} * V_{in} + c_{in}$$

V_{out} digitized by Teensy into ADC:

$$ADC = \frac{4096}{3.3} * V_{out}$$

Solving for V_m and ADC:

$$ADC = \left(\frac{4096 * m_{in} * g_{in}}{3.3} \right) * V_m - \left(\frac{4096}{3.3} \right) * c_{in} \quad (5)$$

Here:

$$\text{Slope } V_m \text{ to ADC} = \left(\frac{4096 * m_{in} * g_{in}}{3.3} \right)$$

And

$$\text{Intercept } V_m \text{ to ADC} = \left(\frac{4096}{3.3} \right) * c_{in}$$

Teensy should know the ADC to V_m conversion. In the dynamic clamp program that goes on the teensy for operation, we need to feed the input slope and input intercept. When we put together the whole board and do calibration, we will change the V_m and record the ADC values from Teensy. From that we will get the "Intercept V_m to ADC" and "Slope V_m to ADC" values. Using that we must obtain the inverse relationship i.e. slope and intercept to get V_m values from ADC values.

$$V_m = \left(\frac{3.3}{4096 * m_{in} * g_{in}} \right) * ADC - \left(\frac{c_{in}}{m_{in} * g_{in}} \right) \quad (6)$$

Here:

$$\text{Input Slope} = \left(\frac{3.3}{4096 * m_{in} * g_{in}} \right) \quad (6a)$$

$$\text{Input Intercept} = \left(-\frac{c_{in}}{m_{in} * g_{in}} \right) \quad (6b)$$

Calculation: Table 4

Quantity	Value	Unit
V _m	-65.00	mV
Gain of Amp		
stage 1	10	x
Stage 2	10	x
Total Input Gain	100	mV/mV
Digitization Max Voltage	3.3	V
Digitization Bit depth	4096	levels
IO relation (from Table 1)	Expected	According to Observed Scaling
Slope V _{out} to V _{in} (m _{in})	0.1599	0.1609
Intercept V _{out} to V _{in} (c _{in})	1.6493	1.6721
V _m to ADC		
Slope V _m to ADC	19.84698182	19.9711
Intercept V _m to ADC	2047.131152	2075.431
Inverse relationship		
Input Slope	0.050385495	0.050072
Input Intercept	-103.1457161	-103.922

Output Stage Calibration

$$V_{AMP} = V_{DC}$$

$$V_{DC} = m_{out} * V_{DAC} + c_{out}$$

$$V_{DAC} = \left(\frac{3.3}{4096} \right) * DAC$$

$$I_{inj} = g_{out} * V_{AMP}$$

Combining all:

$$I_{inj} = \left(\frac{3.3 * m_{out} * g_{out}}{4096} \right) * DAC + (c_{out} * g_{out}) \quad (7)$$

And inversely:

$$DAC = \left(\frac{4096}{3.3 * m_{out} * g_{out}} \right) * I_{inj} + \left(-\frac{4096 * c_{out}}{3.3 * m_{out}} \right) \quad (8)$$

Here:

$$\text{Output Slope} = \frac{4096}{3.3 * m_{out} * g_{out}} \quad (8a)$$

$$\text{Output Intercept} = -\frac{4096 * c_{out}}{3.3 * m_{out}} \quad (8b)$$

During calibration, using processing calibration program with a model cell, the teensy wants to figure out the output relationship i.e., how much DAC value gets converted to how much current injection into the cell. For that, teensy generates an array of DAC values, and then measures the V_m of the model cell (in form of the ADC values). From V_m and resistance of the model cell, it calculates how much current is sent to the model cell.

We have to empirically find Input and Output slopes and intercepts.

Table 5

Quantity	Value	Unit
I_{inj}	-100.00	pA
Total Output Gain	400	pA/V
Digitization Max Voltage	3.3	V
Digitization Bit depth	4096	Levels
IO relation from Table 2	Expected	According to Observed Scaling
Slope (m_{out})	-2.1277	-2.131
Intercept (c_{out})	3.3	3.4485
DAC to I_{inj}		
Slope	-0.68568457	-0.68675
Intercept	1320	1379.4
Inverse relationship		
Output Slope	-1.458396533	-1.45614
Output Intercept	1925.083423	2008.597

Direct Calibration with a Function Generator and an Oscilloscope

In direct calibration, we can give a certain known value on the input side of the stage and measure the value on the output side. From the measurements, if we fit a line, we can get the slope and intercept of that relationship. This can be done using a function generator and an oscilloscope without the need of a model cell.


Input Stage Calibration: $V_{in} \rightarrow \text{ADC}$

Setup:

Put Teensy into circuit. Using a function generator, give known constant voltages to V_{in} and read ADC values recorded by Teensy. Measure the ADC to V_{in} relationship.

Measurement: Table 6, Compare with theoretical values from table 4

Input V_{in} Using a function Gen (V)	Equivalent V_m (mV)	Measured ADC Value
-9	-90	200
-8	-80	402
-7	-70	603
-6	-60	803
-5	-50	1004
-4	-40	1204
-3	-30	1405
-2	-20	1606
-1	-10	1805
0	0	2005
1	10	2206
2	20	2406
3	30	2610
4	40	2810
5	50	3012
6	60	3215
7	70	3419
8	80	3620
9	90	3820
Input Slope	0.0497	
Input Intercept	-99.892	

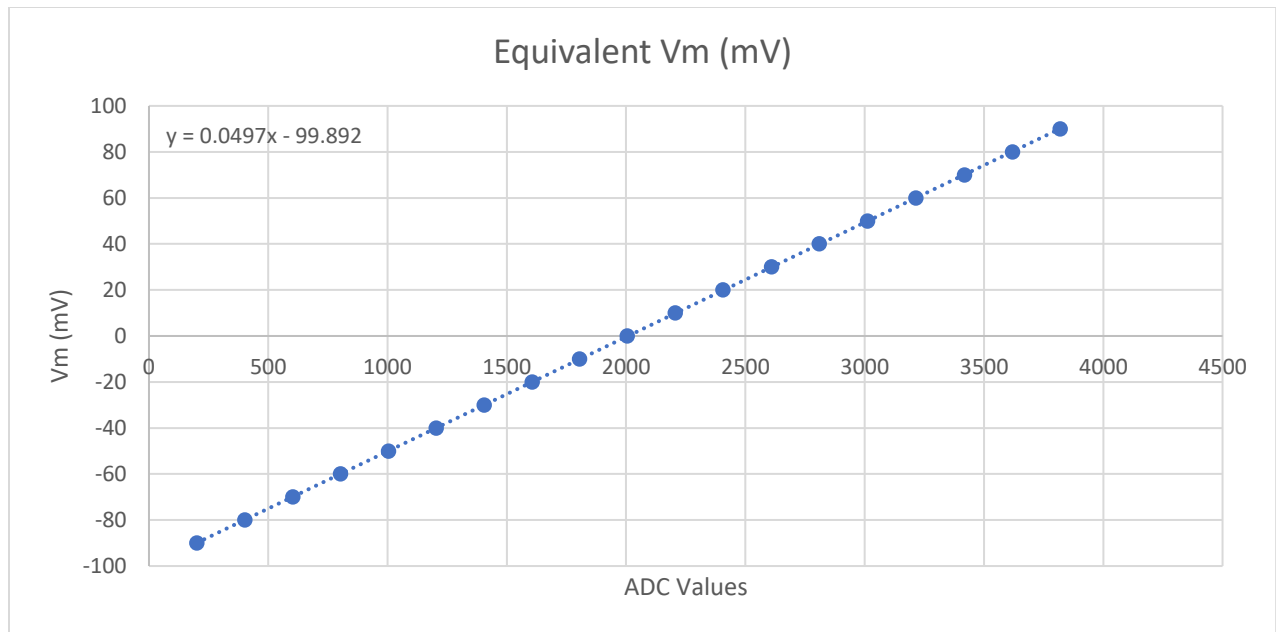


Output Stage Calibration:

Setup: For output calibration, I used a teensy program to give a number of DAC values and recorded the VDAC and VAMP using an oscilloscope. Program script is in appendix.


Measurement: Table 7, Compare with theoretical values from Table 5

i	DAC	VDAC	measured VAMP (V)	I _{inj} (pA) derived from measured VAMP
0	0	0.065	3.31	1324
1	400	0.348	2.65	1060
2	800	0.702	1.96	784
3	1200	1.03	1.28	512
4	1600	1.36	0.583	233.2
5	2000	1.68	-0.095	-38
6	2400	2.01	-0.805	-322
7	2800	2.31	-1.49	-596
8	3200	2.64	-2.18	-872
9	3600	2.96	-2.88	-1152
10	4000	3.3	-3.58	-1432
Output Slope	-1.4489			
Output Intercept	1934.3			

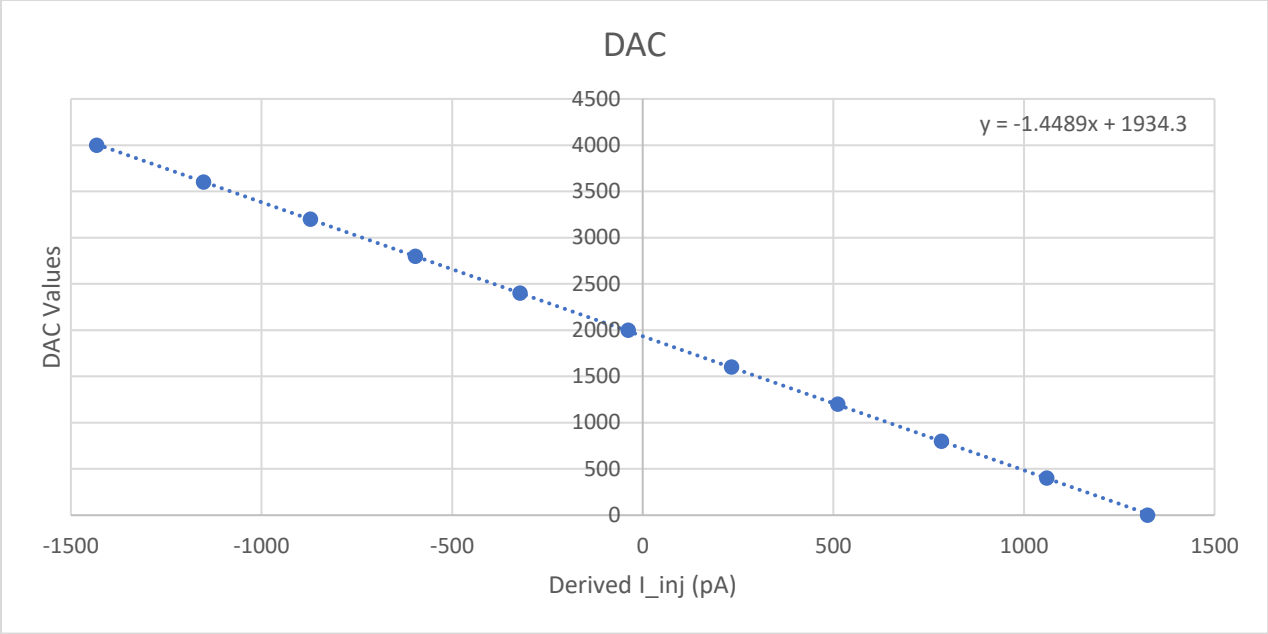

Calibration with a Model Cell Using Processing

Now dynamic clamp can be boxed and put into connection with the Axon devices. Remember the dynamic clamp stage 1 is designed to read a 100x amplified V_m between the range $\pm 10V$. Multiclamp, the patch clamp amplifier sends a secondary output that can be selected to be a scaled copy of membrane potential V_m . It should have the same gain settings of 10, which gives an amplification of 100 mV/mV (i.e., 100x)¹. We will use this output from multiclamp to read cell V_m .

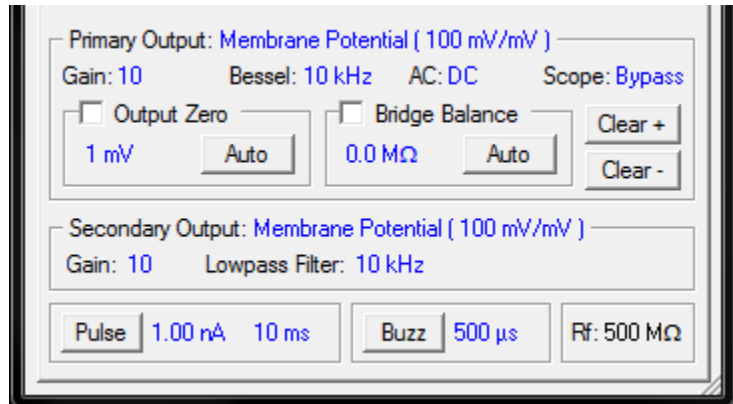

Setup:

Instructions are described in the original documentation. Plug in a model cell, switch to current clamp on multiclamp and remove any offsets so that model cell V_m is 0 mV at 0 pA current injection.

Calibration will be done using the graphical interface written in processing and can be found in the Dynamic Clamp directory. First, we have to upload the *teensy_calibration.ino* file to Teensy and then use Processing program *processing_calibration.pde* to measure input and output slopes and intercepts that we have been doing manually so far.


If you go through the theoretical calibration steps and formulae as described in earlier sections, it will be clear that the calibration values, intercepts, and slopes are entirely a function of resistors and amplifiers used in the circuit and ADC – DAC range of the Teensy and do not depend on the multiclamp amplifier and DAQ.

¹ Multiclamp has an internal gain of 10x that cannot be changed. So, when we select a gain of 10 in the user interface, the actual gain is $10 * 10 = 100$. Refer to table 4.

Input Stage calibration with Processing Program

Table 8


Input Gain	100
V _m (mV)	ADC reading
0.000	2014
-10.800	1803
-31.091	1407
-54.000	960
-80.182	449
80.182	3576
63.818	3255
40.909	2807
20.618	2411
Input Slope	0.0513
Input Intercept	-103.27

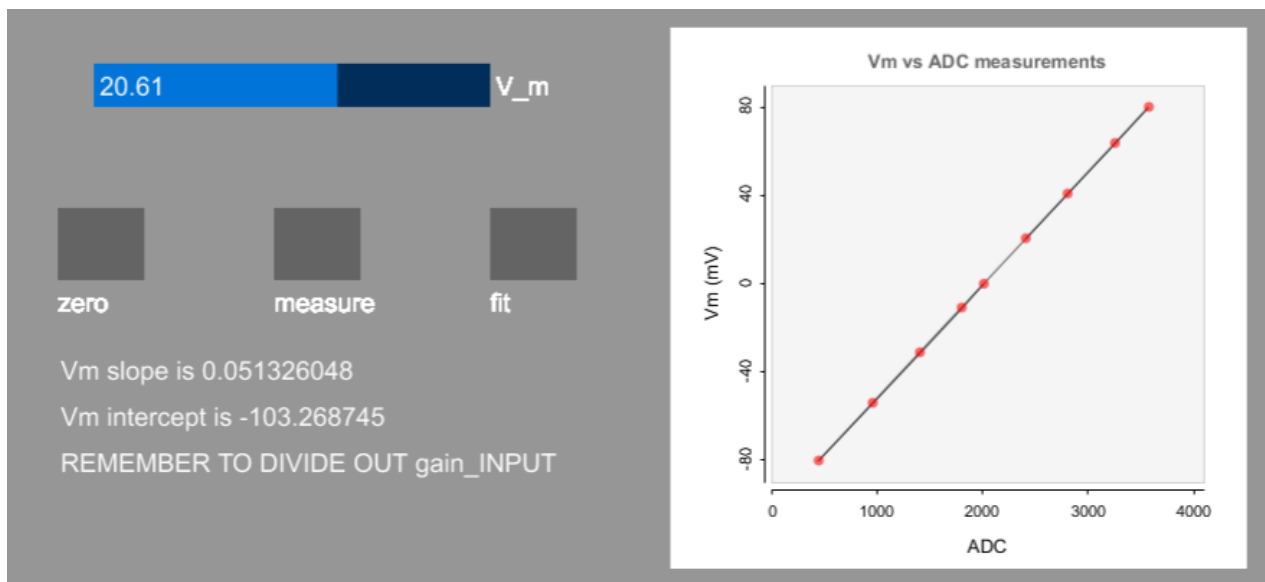

The output of slope and intercept have to be fed into the dynamic clamp main program *dynamic_clamp.ino* after multiplying with the gain (100).

```
50  const float inputslope = 5.13/gain_INPUT.
51  const float inputIntercept = -10327/gain_INPUT.
```

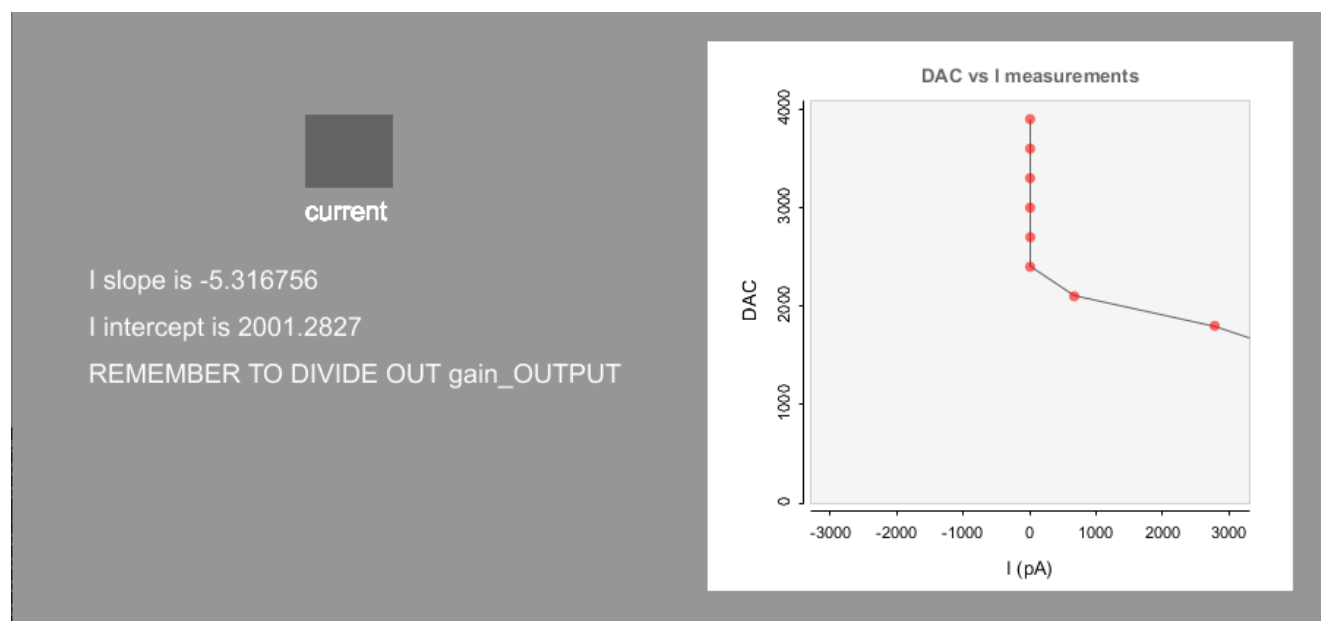Output stage calibration with Processing Program




The processing program generates an error. The reason is that in the backend, the output calibration generates DAC values from 300 to 3900, which in turn would create a VAMP of ± 1.4 nA. The program then measures the V_m , derives I_{inj} from V_m (using user supplied model cell resistance). Normally, for a patched cell ($R_m \sim 100$ M Ω), this current would create a V_m of around ± 100 mV. But when a model cell is used ($R_m \sim 500$ M Ω) the V_m goes beyond 600 mV which is far beyond the range of dynamic clamp input and thus for most of the DAC values, V_m on model cell is unmeasurable.

Table 9: Problem with output slope measurement

DAC	Expected VAMP (approx.)	Corresponding I_{inj}	V_m on Model cell (mV)	V_{in} going into DynClamp (V)	In Range of Teensy? (± 10 V)
0	3.3	1320	671.88	67.188	FALSE
300	2.82	1128	574.152	57.4152	FALSE
600	2.34	936	476.424	47.6424	FALSE
900	1.86	744	378.696	37.8696	FALSE
1200	1.38	552	280.968	28.0968	FALSE
1500	0.9	360	183.24	18.324	FALSE
1800	0.42	168	85.512	8.5512	TRUE
2100	-0.06	-24	-12.216	-1.2216	TRUE
2400	-0.54	-216	-109.944	-10.9944	FALSE
2700	-1.02	-408	-207.672	-20.7672	FALSE
3000	-1.5	-600	-305.4	-30.54	FALSE
3300	-1.98	-792	-403.128	-40.3128	FALSE
3600	-2.46	-984	-500.856	-50.0856	FALSE
3900	-2.94	-1176	-598.584	-59.8584	FALSE
4095	-3.252	-1300.8	-662.107	-66.21072	FALSE

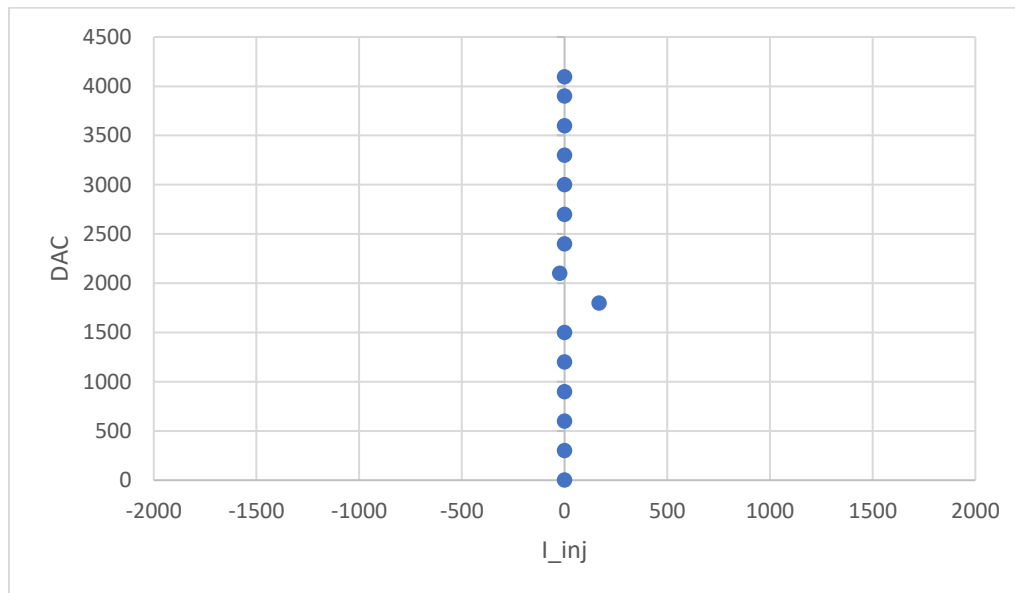Resulting into the above plot or the one below



Solution: Output stage calibration with a Script

There are two ways to solve this problem. Either we can use a model cell with lower resistance, or we can change the range of DAC values that are used in the processing program. There is a bonus method to solve the problem described in the appendix.

Modifying the *processing_calibration.pde* program, line 29-31.

```
// DAC outputs between 300 and 3900 in increments of 300
29 for (int z=0; z<nOutputs; z++) {
30   outputs[z] = 300*(z+1);
31 }
```


Change to:

```
// DAC outputs between 1800 and 2300 in increments of 30
29 for (int z=0; z<nOutputs; z++) {
30   outputs[z] = 1750+30*(z+1);
31 }
```


Note: You may need to tweak the increment value a bit to get a range in which all values come out right. Between 1800 and 2300, we need 13 values as `nOutputs` is fixed at 13, therefore, the right increment would be 30. Do a check, nevertheless.

Table 10: Measurement of output slope and intercept after tweaking the script

DAC	Expected VAMP	Corresponding I _{inj}	V _m on Model cell (mV)	V _{in} going into DynClamp (V)	In Range of Teensy? (±10V)	I _{inj}
1780	0.452	180.8	92.0272	9.20272	TRUE	180.8
1810	0.404	161.6	82.2544	8.22544	TRUE	161.6
1840	0.356	142.4	72.4816	7.24816	TRUE	142.4
1870	0.308	123.2	62.7088	6.27088	TRUE	123.2
1900	0.26	104	52.936	5.2936	TRUE	104
1930	0.212	84.8	43.1632	4.31632	TRUE	84.8
1960	0.164	65.6	33.3904	3.33904	TRUE	65.6
1990	0.116	46.4	23.6176	2.36176	TRUE	46.4
2020	0.068	27.2	13.8448	1.38448	TRUE	27.2
2050	0.02	8	4.072	0.4072	TRUE	8
2080	-0.028	-11.2	-5.7008	-0.57008	TRUE	-11.2
2110	-0.076	-30.4	-15.4736	-1.54736	TRUE	-30.4
2140	-0.124	-49.6	-25.2464	-2.52464	TRUE	-49.6
2170	-0.172	-68.8	-35.0192	-3.50192	TRUE	-68.8
2200	-0.22	-88	-44.792	-4.4792	TRUE	-88
2230	-0.268	-107.2	-54.5648	-5.45648	TRUE	-107.2
2260	-0.316	-126.4	-64.3376	-6.43376	TRUE	-126.4
2290	-0.364	-145.6	-74.1104	-7.41104	TRUE	-145.6

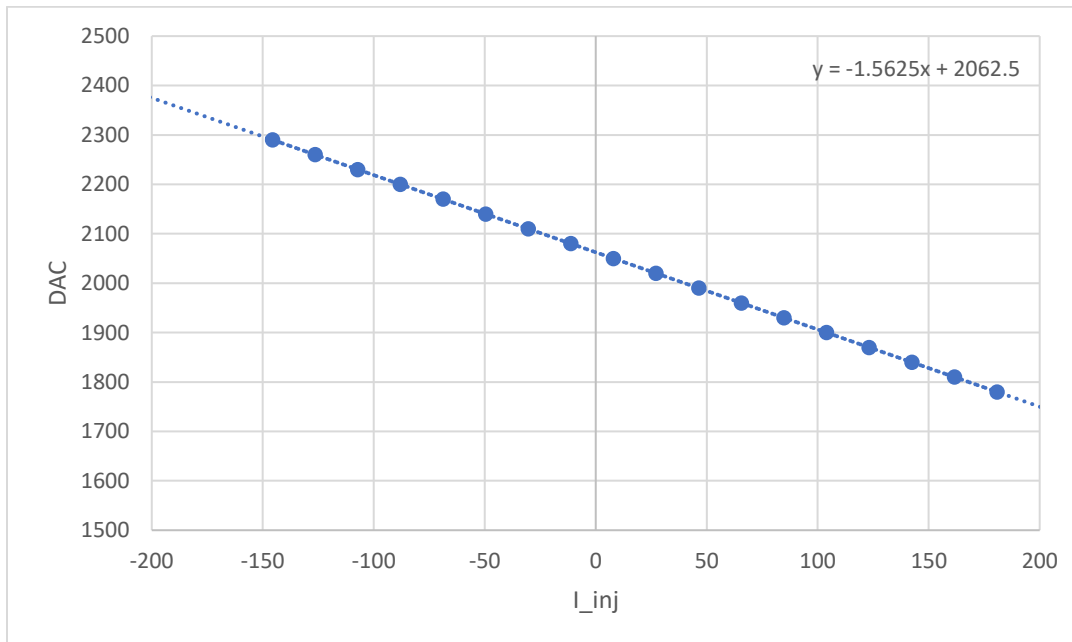

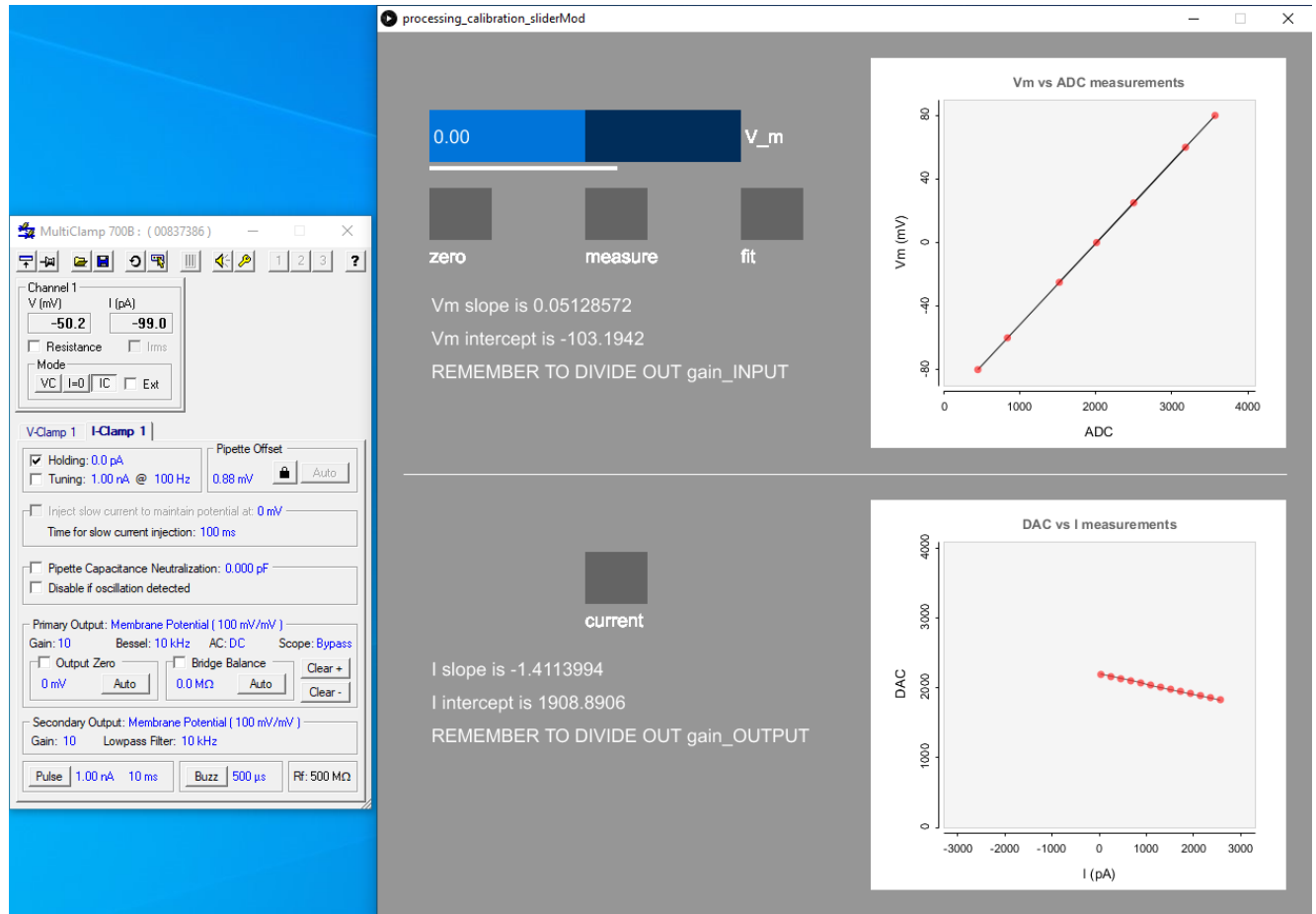Measurement after processing code change:



Note: The fitting values are different from the table as this sample plot is generated from another dynamic clamp setup for demonstration.

Alternative Calibration with a Teensy Program

Another way to measure the input and output slopes and intercepts is to do it manually.


Setup: Script to do that can be found in the appendix.

- i) Change V_m in current clamp in the multiclamp commander, measure ADC values. Plot and fit a line. Get intercept and slope of the fit. These will be input intercept and slope.
- ii) Then, use another script to change DAC values, and measure ADC values. From ADC values get V_m using the relationship obtained in step (i). Get I_{inj} by dividing V_m with model cell resistance. Plot DAC vs I_{inj} . Fit a line and get the slope and intercept values from the fit. These will be your output intercept and slope.

Measurement: Input Calibration


Table 11

ADC	V_m
2075	0
2270	10
2465	20
2660	30
2860	40
3050	50
3245	60
3440	70
3634	80
3832	90
4025	100
1878	-10
1683	-20
1486	-30
1292	-40
1098	-50
903	-60
706	-70
510	-80
315	-90
120	-100
input slope	0.0512
input intercept	-106.17

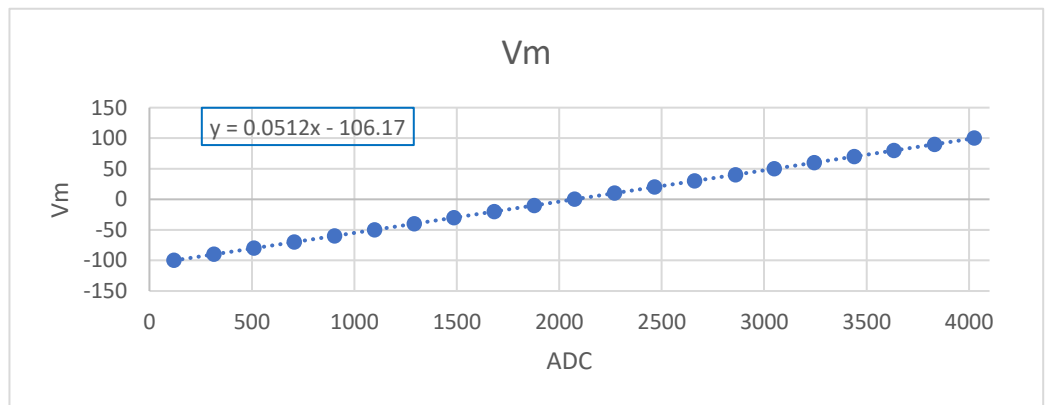

Output Calibration: Table 12

i	DAC	ADC	Multiclamp Vm	Multiclamp Im	Vm	I
0	1650	3844	91	181.9	90.6428	181.7217
1	1675	3674	82.3	164	81.9388	164.2719
2	1700	3504	73.6	146.9	73.2348	146.822
3	1725	3332	64.9	129.7	64.4284	129.1668
4	1750	3162	56.1	111.7	55.7244	111.7169
5	1775	2992	47.4	94.3	47.0204	94.26704
6	1800	2818	38.6	76.4	38.1116	76.40658
7	1825	2654	29.8	59.1	29.7148	59.57257
8	1850	2482	21.1	41.5	20.9084	41.9174
9	1875	2312	12.4	24.7	12.2044	24.46752
10	1900	2142	3.6	6.6	3.5004	7.017642
11	1925	1969	-5.2	-11.1	-5.3572	-10.7402
12	1950	1798	-13.9	-28.5	-14.1124	-28.2927
13	1975	1629	-22.6	-45.9	-22.7652	-45.6399
14	2000	1459	-31.3	-63.5	-31.4692	-63.0898
15	2025	1288	-40	-81.2	-40.2244	-80.6423
16	2050	1118	-48.8	-98.6	-48.9284	-98.0922
17	2075	945	-57.6	-116.1	-57.786	-115.85
18	2100	776	-66.3	-133.8	-66.4388	-133.197
19	2125	607	-75	-151.8	-75.0916	-150.545
20	2150	437	-83.8	-168.6	-83.7956	-167.994
21	2175	267	-92.5	-186.2	-92.4996	-185.444
22	2200	97	-101.2	-203.6	-101.204	-202.894
Output Slope		-1.4295				
Output Intercept		1909.8				

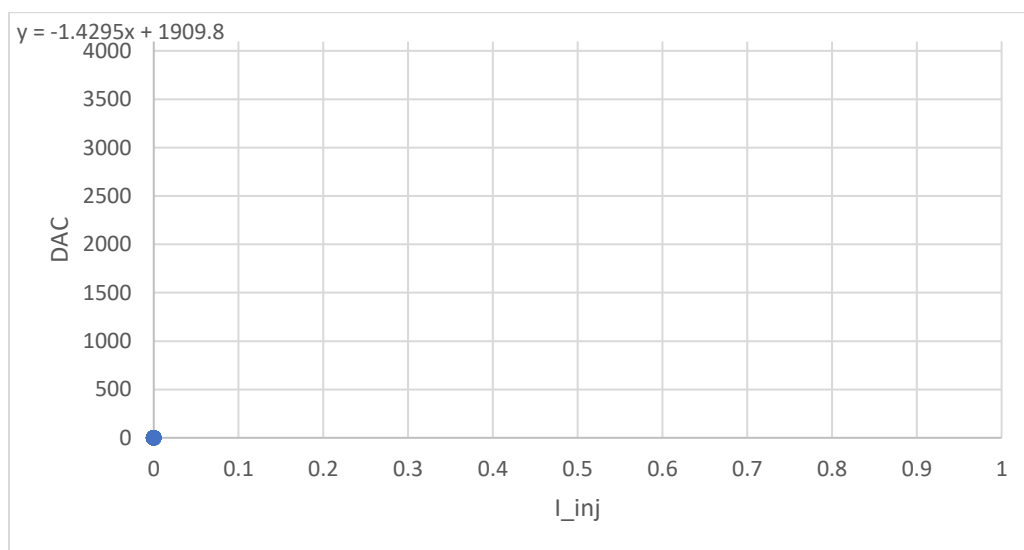

Conclusion

The whole objective of all the step by step and stage-by stage exercise was to finally, determine the relationship between what Dynamic Clamp measures and what Dynamical Clamp maps it to. It has to map the readout on it is pin 0, i.e., ADC to V_m and also map its output from DAC onto the injected current I_{inj} .

In the dynamic clamp setup that was made along with the writing of this manual, the input-output intercepts and slopes came out to be:

Table 13

Input Slope	0.0513
Input Intercept	-103.27
Output Slope	-1.4321
Output Intercept	1913.6

Finally, we have to put these values into the *dynamic_clamp.ino* file.

Summary of Values, errors in different measurements:

Either of the green shaded column values can be used.

	Theoretical	Expected From Individual Modules	Direct From Individual Modules with Function Gen	Whole Setup with Processing GUI and Model Cell	Whole Setup Direct with Code and Model Cell	% Error Between Theoretical and Direct with Code
Input Slope	0.050	0.050	0.050	0.051	0.051	1.617
Input Intercept	-103.146	-103.922	-99.892	-103.270	-106.170	2.932
Output Slope	-1.458	-1.456	-1.449	-1.432	-1.430	-1.981
Output Intercept	1925.083	2008.597	1934.300	1913.600	1909.800	-0.794

Feeding the calibration values in Dynamic Clamp

The input and output intercepts and slopes obtained in sections above and summarized in the last section need one more modification before being put into the dynamic clamp program. Recall from Equation 6 and Table 13 for input that:

$$\text{Input Slope} = \left(\frac{3.3}{4096 * m_{in} * g_{in}} \right) = 0.0513$$

And

$$\text{Input Intercept} = \left(-\frac{c_{in}}{m_{in} * g_{in}} \right) = -103.27$$

As one can see, both quantities are dependent on amplifier input gain g_{in} . To make the code more general to be used with different values of input gain, we can take g_{in} out and use it as another variable.

$$\text{Input Slope} = \left(\frac{3.3}{4096 * m_{in} * g_{in}} \right) = \frac{5.13}{g_{in}}$$

And

$$\text{Input Intercept} = \left(-\frac{c_{in}}{m_{in} * g_{in}} \right) = -\frac{10327}{g_{in}}$$

Similary, to make the dynamic clamp code more general to be used with different values of g_{out} , we need to factor out g_{out} from equations 8a and 8b.

$$\text{Output Slope} = \frac{4096}{3.3 * m_{out} * g_{out}} \quad (8a)$$

$$\text{Output Intercept} = -\frac{4096 * c_{out}}{3.3 * m_{out}} \quad (8b)$$

From 8b, we can see the output intercept does not depend on g_{out} . The final value from 8a and Table 13:

$$\text{Output Slope} = \frac{4096}{3.3 * m_{out} * g_{out}} = -\frac{1.430 * 400}{g_{out}} = \frac{572}{g_{out}}$$

$$\text{Output Intercept} = -\frac{4096 * c_{out}}{3.3 * m_{out}}$$

Rest all constants, m_{in} , m_{out} , c_{in} , c_{out} , 4096, and 3.3 are property of the circuit and are not changeable from outside.

Feed the final values in *Dynamic_Clamp.ino* file:

```
50 const float inputSlope = 5.12/gain_INPUT;
51 const float inputIntercept = -10617/gain_INPUT;
52 const float outputSlope = -571.8/gain_OUTPUT;
53 const float outputIntercept = 1909.8;
```

Appendix

Script for alternative calibration using a Teensy program

```
//+++++
/*
  Analog input, analog output, serial output
  Aditya Asopa, Bhalla lab, NCBS Oct 2020
*/

// These constants won't change. They are used to give names to the pins
used:
// Analog input pin that the Vm is read from
const int analogInPin = A0;
// Analog output pin that the DAC goes out from
const int analogOutPin = A21;

int sensorValue = 0;      // value read from the ADC
int outputValue = 0;      // value output to the DAC

void setup() {
  // initialize serial communications at 115200 bps:
  Serial.begin(115200);
  analogWriteResolution(12);
  //very important to set the bit resolution
  analogReadResolution(12);
}
/*Teensy cant read any value of Vm that is beyond +/-100mV.
 * Since the model cell has a resistance of 500MΩ, a Vm of 100mV is
produced with a current of 200pA.
 * Therefore, IDC has to be between +/- 200pA.
 * For that, corresponding DAC has to be between 1800 - 2300 (check the
previous sheet for scaling).
 * Therefore, the right range of DAC to give here is 1750 to 2300.
 */
void loop() {
  for (int i = 0; i <= 20; i++) {
    //outputSlope * injectionCurrent + outputIntercept;
    int Iinj = i*30+1750;
    // make sure the output is an integer between 0 and 4095 (12 bits)
    int DAC = constrain((int)Iinj,0,4095);
    analogWrite(analogOutPin,DAC);
    delay(1000);
    int adc = analogRead(analogInPin);
```

```
    Serial.println(i);
    Serial.print("\t");
    Serial.print(DAC);
    Serial.print("\t");
    Serial.print(adc);
    delay(1000);
}
}
//+++++
```


Bonus method to solve the output calibration problem with the processing calibration program

As described in the section, the problem arises due to huge resistance of the model cell, the Vm drop after amplification goes out of the range of Teensy ADC. We can therefore also solve the problem by changing not the resistance of model cell but by changing the gain of the amplifier and then factoring it back in (recall Eq. 8)

Steps:

1. Keep the input gain at 10 (100mV/mV). Measure the input slope and intercept like usual.
2. Change the gain to 1 (10 mV/mV). Run the output stage calibration.
3. Factor back the gain into the calculation before plugging into dynamic clamp program.

Sample result:

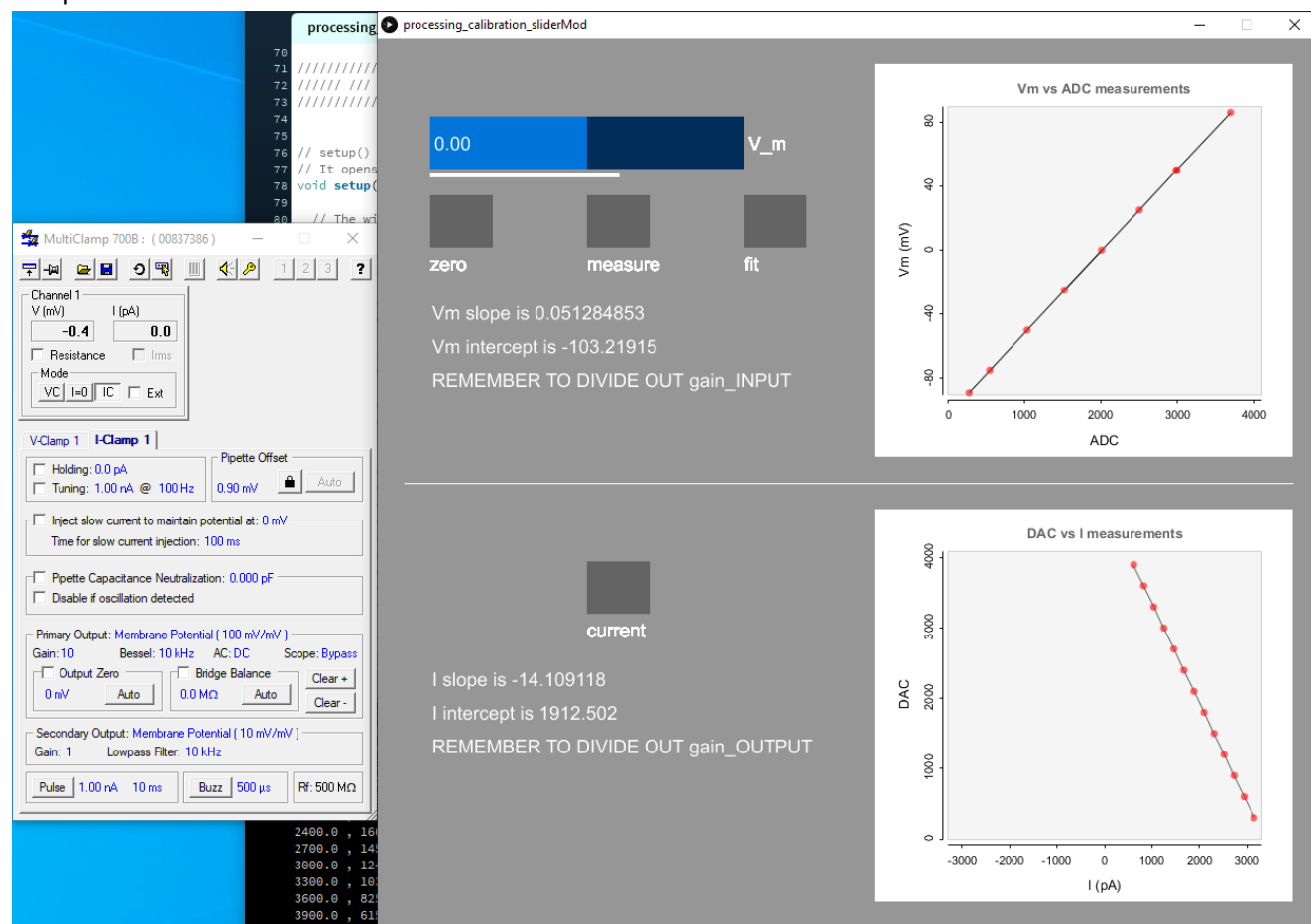

So, the correct output values to be put into the *dynamic_clamp.ino* program will be:

Output slope = $-1.410911/g_{out}$ and

Output intercept = 1912.502

See if you can figure out why output slope had to be divided by 10 and intercept was left as is. Hint: input gain.